

Name: _____ Date: _____

1. What is included in a complete electrical circuit?
 - A. A power source
 - B. A resistor
 - C. A capacitor
 - D. A diode

2. What is the difference between a short-to-voltage and a short-to-ground?
 - A. Location of the short
 - B. Resistance value
 - C. Voltage drop
 - D. Current flow

3. Which of the following is NOT a feature of a short circuit?
 - A. It involves the power side of the circuit.
 - B. It involves a copper-to-copper connection.
 - C. It always results in a blown fuse.
 - D. It is a complete circuit.

4. What does Ohm's law help determine if the voltage (E) and resistance (R) are known?
 - A. Power
 - B. Frequency
 - C. Current (I)
 - D. Capacitance

5. Which of the following is a unit of electrical power?
 - A. Ohm
 - B. Volt
 - C. Ampere
 - D. Watt

6. How many watts are consumed by a lightbulb if 1.2 amperes are measured when 12 volts are applied?
 - A. 14.4 watts
 - B. 144 watts
 - C. 10 watts
 - D. 0.10 watt

7. High resistance in an electrical circuit can cause:
 - A. Dim lights
 - B. Slow motor operation
 - C. Clicking of relays or solenoids
 - D. All of the above

8. If the voltage increases in a circuit, what happens to the current (amperes) if the resistance remains the same?

- A. Increases
- B. Decreases
- C. Remains the same
- D. Cannot be determined

9. If 200 amperes flow from the positive terminal of a battery and operate the starter motor, how many amperes will flow back to the negative terminal of the battery?

- A. Cannot be determined
- B. Zero
- C. One half (about 100 amperes)
- D. 200 amperes

10. What is the symbol for voltage used in calculations?

- A. R
- B. E
- C. EMF
- D. I

Automotive Technology 7th Edition

Chapter 37

Multiple Choice Quiz A

Answer Key

1. A

2. A

3. C

4. C

5. D

6. A

7. D

8. A

9. D

10. B