

Name: \_\_\_\_\_ Date: \_\_\_\_\_

1. Which circuit failure is most likely to cause the fuse to blow?

- A. Open
- B. Short-to-ground
- C. Short-to-voltage
- D. High resistance

2. What happens when a power path wire accidentally touches a return path wire or conductor?

- A. Short-to-voltage
- B. Open circuit
- C. Short-to-ground
- D. High resistance

3. What is the result of a short-to-ground in a circuit?

- A. Increased voltage
- B. Blown fuse
- C. Increased resistance
- D. Decreased current

4. What is the relationship between current (amperes) and voltage (potential) in a circuit?

- A. As current increases, voltage decreases.
- B. As current decreases, voltage increases.
- C. Current and voltage are not related.
- D. Current and voltage are directly proportional.

5. What is the primary purpose of a fuse in an electrical circuit?

- A. To increase voltage
- B. To decrease resistance
- C. To prevent possible overheating damage in the event of a short circuit
- D. To amplify the current

6. What is the result of a short circuit in which the current bypasses some or all of the resistance?

- A. Increased resistance
- B. Decreased voltage
- C. Increased voltage
- D. Decreased resistance

7. What is the primary purpose of an electrical switch in a circuit?

- A. To increase voltage
- B. To decrease resistance
- C. To open or close the circuit
- D. To amplify the current

8. Which of the following is NOT a cause of an open circuit?

- A. Broken wire
- B. Blown fuse
- C. Short-to-ground
- D. Corroded connection

9. What is the relationship between power (watts), current (amperes), and voltage (volts) in a circuit?

- A.  $P = I * E$
- B.  $P = I / E$
- C.  $P = E / I$
- D.  $P = I + E$

10. What is the result when a circuit is not complete or lacks continuity?

- A. Short-to-voltage
- B. Open circuit
- C. Short-to-ground
- D. High resistance

Automotive Technology 7th Edition

Chapter 37

Multiple Choice Quiz B

Answer Key

1. B

2. C

3. B

4. A

5. C

6. D

7. C

8. C

9. A

10. B