

Name: _____

Date: _____

1. Which type of circuit has more than one electrical load where all of the current has only one path to flow through all of the loads?

- A. Parallel circuit
- B. Series circuit
- C. Series-parallel circuit
- D. Compound circuit

2. In which type of circuit is the total resistance the sum of the individual resistances?

- A. Parallel circuit
- B. Series circuit
- C. Series-parallel circuit
- D. Compound circuit

3. Which law states that the current is constant throughout the entire circuit?

- A. Ohm's law
- B. Kirchhoff's voltage law
- C. Kirchhoff's current law
- D. Faraday's law

4. What is the term used to describe the voltage reduction that occurs when current flows through a resistance?

- A. Voltage surge
- B. Voltage drop
- C. Voltage spike
- D. Voltage deviation

5. In a parallel circuit, if there is more than one path for the current to flow, most of the current will flow through the branch with the _____.

- A. Lowest resistance
- B. Highest resistance
- C. Highest voltage
- D. Lowest voltage

6. Which of the following is NOT considered to be included in the determination of a series circuit?

- A. Fuses
- B. Motors
- C. Bulbs
- D. Resistors

7. What happens to the current in a series circuit if there is a break (open) anywhere in the circuit?

- A. It doubles
- B. It reduces by half
- C. It remains constant
- D. It stops

8. In a series-parallel circuit problem, what is the key to simplification?

- A. Multiply resistances first
- B. Subtract resistances first
- C. Combine or simplify resistances as much as possible
- D. Divide resistances first

9. Which law states that the sum of the individual voltage drops in a series circuit is equal to the total applied voltage?

- A. Ohm's law
- B. Kirchhoff's voltage law
- C. Kirchhoff's current law
- D. Faraday's law

10. In a parallel circuit where there is more than one path for the current to flow, where does the majority of the current flow?

- A. Through the path with the lowest resistance
- B. Through the path with the highest resistance
- C. Equally through all paths
- D. Through the path closest to the power source

Automotive Technology 7th Edition

Chapter 38

Multiple Choice Quiz A

Answer Key

1. B

2. B

3. C

4. B

5. A

6. A

7. D

8. C

9. B

10. A