

Name: _____

Date: _____

1. When a capacitor is placed in a closed circuit, what happens to the voltage source?
 - A. It decreases.
 - B. It remains constant.
 - C. It forces electrons around the circuit.
 - D. It gets discharged.

2. What is the primary function of a capacitor in noise filtering?
 - A. To amplify the noise.
 - B. To store the noise.
 - C. To block the flow of direct current (DC).
 - D. To allow AC to pass.

3. The larger the surface area of the plates of a capacitor, the _____ the capacitance.
 - A. Smaller
 - B. Greater
 - C. Unchanged
 - D. More variable

4. What happens when a capacitor is electrically charged in a computer memory?
 - A. It represents the binary digit 0.
 - B. It represents the binary digit 1.
 - C. It erases the memory.
 - D. It amplifies the signal.

5. In what type of memory is a capacitor primarily used?
 - A. Static random-access memory (SRAM)
 - B. Read-only memory (ROM)
 - C. Dynamic random-access memory (DRAM)
 - D. Flash memory

6. What is the primary purpose of the dielectric in a capacitor?
 - A. To conduct electricity between the plates.
 - B. To store electrical charge.
 - C. To insulate and prevent the flow of electricity between the plates.
 - D. To amplify the current.

7. When a capacitor is placed in a circuit, and the voltage source forces electrons around the circuit, what happens to the electrons?
 - A. They flow through the dielectric.
 - B. Excess electrons collect on the negatively charged plate.
 - C. They get neutralized.
 - D. They get stored in the battery.

8. What was the primary discovery made using the Leyden jar?

- A. A charge could be stored for a period of time.
- B. Electricity could be amplified.
- C. Resistance could be measured.
- D. Voltage could be increased.

9. In a capacitor, what happens when the negative plate and the negative terminal of the battery are at the same negative potential?

- A. The circuit is in balance, and there is no current.
- B. The circuit gets short-circuited.
- C. The capacitor discharges.
- D. The capacitor gets damaged.

10. What is the primary purpose of a capacitor in timer circuits?

- A. To amplify the current.
- B. To store energy and allow it to discharge through a resistance load.
- C. To block the flow of current.
- D. To act as a switch.

Automotive Technology 7th Edition

Chapter 43

Multiple Choice Quiz B

Answer Key

1. C

2. D

3. B

4. B

5. C

6. C

7. B

8. A

9. A

10. B