

# Parallel Circuits

## Chapter 7

