

**Automotive Electrical and Engine Performance 9th Edition**  
**Chapter 4 – Series, Parallel, and Series-Parallel Circuits**  
**Multiple Choice Questions Quiz B**

1. In a series circuit, the total resistance is calculated by:
  - a) Dividing the sum of the resistances by the total current
  - b) Multiplying the resistance values of each component
  - c) Adding the resistance values of each component
  - d) Subtracting the lowest resistance from the highest
  
2. Technician A says that an open in any part of a series circuit will stop current flow entirely. Technician B says that an open will only reduce current flow. Who is correct?
  - a) Technician A only
  - b) Technician B only
  - c) Both Technicians A and B
  - d) Neither Technician A nor B
  
3. According to Kirchhoff's Voltage Law in a series circuit:
  - a) The sum of the current at each junction is zero
  - b) The sum of all voltage drops is equal to the total voltage applied
  - c) Total resistance equals the total current times voltage
  - d) Voltage is divided equally across all resistances
  
4. What effect does adding another resistor in series have on the total circuit resistance?
  - a) It decreases the total resistance
  - b) It has no effect on total resistance
  - c) It increases the total resistance
  - d) It doubles the total current flow

5. In a parallel circuit, if one branch opens, the remaining branches:

- a) Lose all current flow
- b) Continue to conduct based on their own resistance values
- c) Share the voltage drop equally
- d) Double the current flow

6. Technician A states that current is the same at every point in a series circuit. Technician B says voltage is the same across each resistor in a series circuit. Who is correct?

- a) Technician A only
- b) Technician B only
- c) Both Technicians A and B
- d) Neither Technician A nor B

7. A parallel circuit with resistances of 4 ohms and 12 ohms will have a total resistance that is:

- a) Higher than the lowest resistance
- b) Lower than the lowest resistance
- c) Equal to the highest resistance
- d) Equal to the sum of all resistances

8. In a series-parallel circuit, a fault in the series portion of the circuit affects:

- a) Only the parallel branches
- b) All parts of the circuit
- c) The ground path only
- d) The circuit's voltage source

9. Kirchhoff's Current Law states that the total current entering a junction in a parallel circuit:

- a) Equals the sum of currents leaving the junction
- b) Is halved across each path
- c) Is inversely proportional to resistance
- d) Doubles across each path

10. When solving a series-parallel circuit, the initial step is typically to:

- a) Identify and combine series resistances within parallel branches
- b) Measure total voltage at each branch
- c) Calculate total current flow first
- d) Adjust resistances to equal values

**Automotive Electrical and Engine Performance 9th Edition**  
**Chapter 4 – Series, Parallel, and Series-Parallel Circuits**  
**Answer Key Quiz B**

**Correct Answers:**

1. c
2. a
3. b
4. c
5. b
6. a
7. b
8. b
9. a
10. a