

Automotive Technology 7th Edition
Chapter 42: Wiring Schematics and Circuit Testing
Short Answer Quiz

Name: _____ Date: _____

1. Explain the significance of the circuit numbers shown on schematics.

2. Describe the function and importance of terminal numbers on an ISO relay.

3. How does a tone generator assist in locating a short circuit?

4. Differentiate between a relay and a solenoid in terms of their functions and applications.

5. What are the steps involved in the circuit troubleshooting procedure?

Automotive Technology 7th Edition
Chapter 42: Wiring Schematics and Circuit Testing
Short Answer Quiz

Name: _____ Date: _____

6. Discuss the importance of connectors in electrical circuits and how they are typically labeled on schematics.

7. How can color-coding parts of a circuit assist in diagnosing system faults?

8. Describe the role of a "Wiggle Test" in identifying intermittent electrical problems.

9. Explain the difference between an earth ground symbol and a chassis ground symbol in electrical schematics.

10. What are the typical electrical and electronic symbols used in automotive wiring and circuit diagrams, and why are they important?
