

**Answer Key**

1. mechanical
2. battery
3. positive
4. alternator
5. ignition (or charging)
6. not running (or off)
7. magnetic
8. switched
9. voltage regulator
10. ignition light (or warning lamp)