

Answer Key

1. ECM (or Engine Control Module / control module)
2. interlocks
3. 5 (or five)
4. resistor
5. voltage
6. 0 (or zero)
7. 1 (or one)
8. 2 (or two)
9. series
10. maximum (or highest)