Online Assignment

Chapter 40
Electrical Circuits and Ohm's Law

Question 3

(Online) find articles and/or videos about short-to-voltage and short-to-ground. (Below) list the difference between short-to-voltage and short-to-ground. List one example for each short-to-voltage and short-to-ground that a technician may find on a vehicle. Be prepared for in-class discussion. List references.

Copyright 2020 James Halderman