Online Assignment

Chapter 41
Series, Parallel, and Series-Parallel Circuits

Question 1

(Online) find articles and/or videos on vehicle series and parallel circuits. (Below) list the difference between series and parallel circuits. List one example for each type of circuit that a technician may find on a vehicle. Be prepared for in-class discussion. List references.

Copyright 2020 James Halderman