Online Assignment

Chapter 41
Series, Parallel, and Series-Parallel Circuits

Question 2

(Online) find articles and/or videos calculating total resistance across a series circuit. (Below) list one example of a series circuit calculation. List the formula used to complete the calculation and list the total resistance. List why calculating total series circuit resistance is important to technicians. Be prepared for in-class discussion. List references.

HALDERMAN
WWW.JAMESHALDERMAN.COM
Copyright 2020 James Halderman