# Online Assignment

## Chapter 41
## Series, Parallel, and Series-Parallel Circuits

### Question 4

(Online) find articles about vehicle series-parallel circuits. (Below) list the definition for series-parallel circuits. List several components were a technician may find series-parallel circuits. Be prepared for in-class discussion. List references.


Copyright 2020 James Halderman