

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

1) Electron A) Digital meter 1) _____


2) 1 to 3 valence electrons B) A conductor 2) _____

3) Measure of current flow C) Class A 3) _____

4) EMF D) Voltage 4) _____


5) Has a probe and small bulb E) Light emitting diode 5) _____

6) Open circuit F) Negative charge 6) _____

7)  G) Connector 7) _____

8) Low speed network H) Relay 8) _____

9) Measures voltage I) Test light 9) _____

10)  J) Metal terminal 10) _____

11) Makes an electrical connection K) Fuse 11) _____

12) An electromagnetic switch L) Ampere 12) _____

13)  M) Lamp 13) _____

14)  N) No current flow 14) _____

Answer Key

Testname: ATT7_MATCH8

- 1) F
Page Ref: 107
- 2) B
Page Ref: 106
- 3) L
Page Ref: 110
- 4) D
Page Ref: 110
- 5) I
Page Ref: 115
- 6) N
Page Ref: 111
- 7) E
Page Ref: 113
- 8) C
Page Ref: 127
- 9) A
Page Ref: 116
- 10) G
Page Ref: 112
- 11) J
Page Ref: 120
- 12) H
Page Ref: 123
- 13) M
Page Ref: 113
- 14) K
Page Ref: 113