

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

1) Senses coolant temperature


A) Temp sensor circuit

1) _____

2) Located in the intake duct

B) PCM advances timing

2) _____

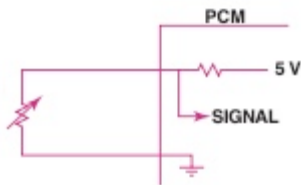

C) IAT sensor

3)

D) Idle control circuit

E) -40°C

3) _____

4) Located inside the transmission


F) NTC sensor

4) _____

5) TFT over 260°F

G) TFT sensor

5) _____

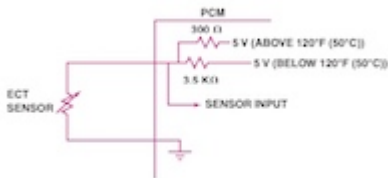

H) Stepped ECT circuit

6)

I) Turns on transmission cooler

J) PCM adds fuel

6) _____

7) Temp up/resistance down

K) Disables overdrive

7) _____

8) Unplugged ECT

L) ECT sensor

8) _____

9) Air temperature low

M) PCM subtracts fuel

9) _____

10) Air temperature high

10) _____

Answer Key

Testname: AEEP8_MATCH31

1) L

Page Ref: 503

2) C

Page Ref: 509

3) A

Page Ref: 511

4) G

Page Ref: 511

5) K

Page Ref: 512

6) H

Page Ref: 504

7) F

Page Ref: 503

8) E

Page Ref: 509

9) J

Page Ref: 509

10) M

Page Ref: 509