Online Assignment

Chapter 41
Series, Parallel, and Series-Parallel Circuits

Question 3

(Online) find articles or videos about Kirchhoff's current law (Below) answer the question: does the sum of the currents entering a junction equal the sum of the currents leaving the junction. List how understanding Kirchhoff's current law is important to technicians working on a vehicle's electrical system. Be prepared for in-class discussion. List references.

HALDERMAN
WWW.JAMESHALDERMAN.COM
Copyright 2020 James Halderman